

We noticed you're visiting from Austria. We've updated our prices to Euro for your shopping convenience. Use United States (US) dollar instead. [Dismiss](#)


[Design Blog](#) [Embedded](#)

ESP32 CP2102 PROGRAMMER SCHEMATIC

ESP32 CP2102 programmers are very common in the market. You can find them in almost any hobby store online. However, sometimes it really helps to integrate the programmer section into your application design – be it development boards or final products. A circuit like this can safely allow the user to upgrade firmware of the product with no risk of “bricking” it. In high volume production runs, adding the ESP32 CP2102 programmer block adds to BoM cost by barely a dollar.

Also, you can use this CP2102 schematic to make an ESP8266 programmer.

ESP32 CP2102 Programmer Schematic

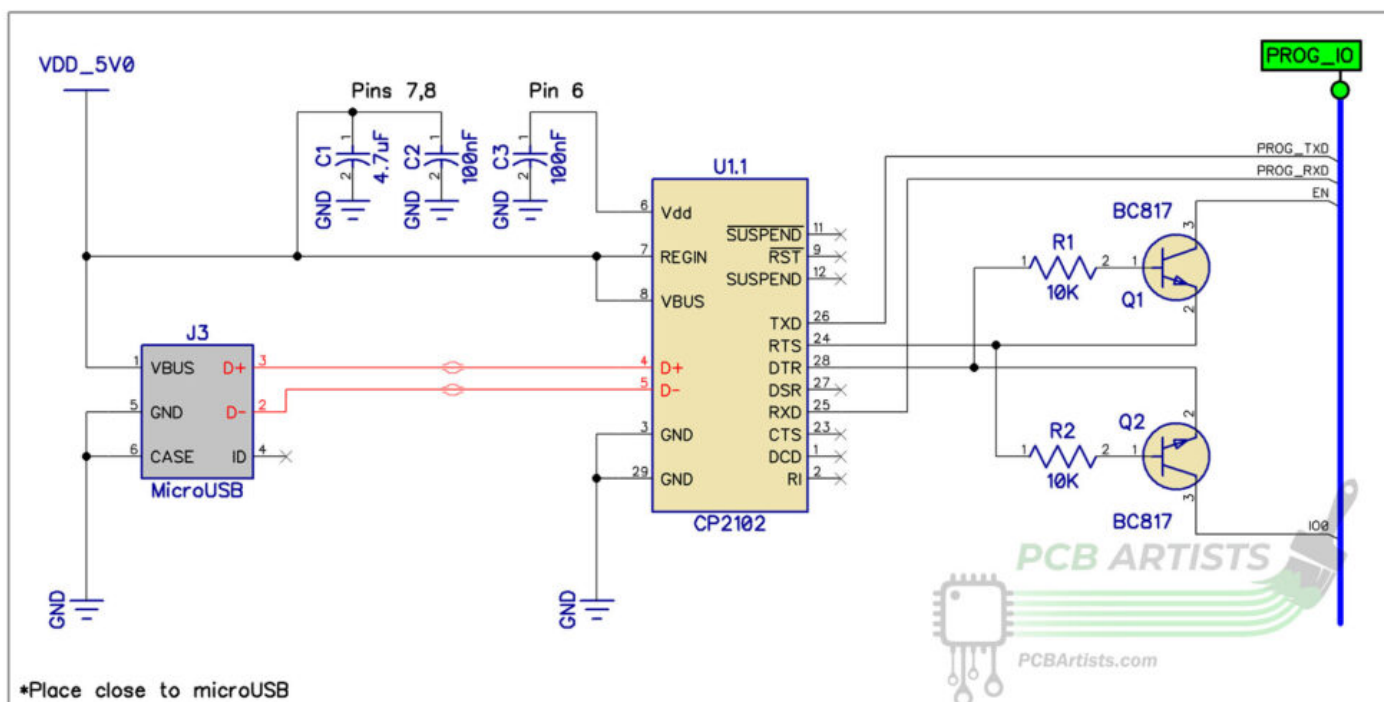



Left to right, the above schematic contains a USB connector. It could be any regular mini-USB or micro-USB connector, they all have similar pinouts.



The USB type C connectors will have more pins, we are not getting into type C connector based schematics in this post, but you can [easily use a USB type-C connector](#) instead of the usual micro-USB

CP2102 power configuration options

In the programmer schematic presented above, the CP2102 is configured to **bus-powered mode**. In this bus-powered mode, the chip gets its power from the USB port.

About using bus-powered configuration:

- This configuration is suitable for cases where you want the CP2102 to activate only when the USB connector is plugged in. If your application is powering the ESP32 or ESP8266 from another source such as a LiPo battery pack, this mode is the one you should use. That will ensure that the CP2102 does not run your battery down for no reason.
- Note that the total capacitance on the USB power lines should be **4.7uF or less** in typical applications. This is to ensure that the short circuit or overcurrent protection inside the USB host does not trip up when the decoupling caps draw a surge of current on connection.
- If the rest of the circuit uses power from the same USB port, make sure you account for the total power consumption and keep it under the maximum specified USB host current capability.

About using self-powered configuration:

- This configuration is suitable when you have a mains powered application or an application where power consumption is not very relevant to you. You can connect REGIN pin of CP2102 to this power source (consult the datasheet for voltage limitations). VDD and REGIN can also be tied together so the circuit can provide a well filtered 3.3V.
- VBUS should still connect to the USB connector power pin so that the CP2102 can enumerate when it detects presence of a physical USB connection.

How auto-program circuit works when programming ESP32 or ESP8266



Here is a table of the pin states and corresponding EN and IO0 levels, assuming that IO0 and EN are pulled up in the ESP32 or ESP8266 system being programmed:

| RTS | DTR | IO0 | EN |
|------|------|------|------|
| Low | Low | High | High |
| Low | High | High | Low |
| High | Low | Low | High |
| High | High | High | High |

The above table might confuse you a little, because it cannot pull both IO0 and EN low at the same time (which is needed for changing modes on the ESP32 or ESP8266). The secret to that is the **capacitance on the EN pin** that is required in all circuits.

Make sure that you have at least 0.1uF capacitance on the EN pin for this auto-programmer circuit to work reliably.

When there is sufficient capacitance on the EN pin to hold it low for a while, the programmer pulls IO0 and by the time the EN pin rises, the ESP reads a low level on IO0 and boots into programming mode. Clever little trick?

EN pin should have at least 100nF of capacitance EN pin needs capacitor of at least 100nF and a pull of at least 10K for auto-program circuit to work!

Change Log

- **Initial Release:** 17 October 2020

References



▪ Reference 3: ESP32-DevKitC schematics

[CONTACT US](#)[STORE](#)[CP2102](#)[ESP32](#)[ESP8266](#)[PROGRAMMER](#)[SCHEMATIC](#)

2 comments

0



YOU MAY ALSO LIKE

GETTING STARTED WITH ARDUINO
AND ESP32

STM32 WIFI – WHAT ARE YOUR
OPTIONS?

“ERROR: SIM FAILURE” IN SIM
4G LTE MODEMS...



LEAVE A COMMENT

Your Comment

Name*

Email*

Website

☐ Save my name, email, and website in this browser for the next time I comment.

Please enter an answer in digits:



2 COMMENTS

ALEJANDRO GUIRAO

🕒 February 10, 2023 - 5:06 pm

According to the datasheet of the CP2102N (<https://www.mouser.de/datasheet/2/368/cp2102n-datasheet-1082647.pdf>) VBUS must be connected with a voltage divider to the power supply your wiring above you could damage the CP2102N or do I misinterpret the datasheet?

PRATIK (A PCBARTIST)

🕒 February 11, 2023 - 11:58 am

The schematic above is based on a CP2102, not a CP2102N! The 2102N series has different IO voltage levels.

From a quick look at the CP2102N datasheet, I think what they mean to say is that the VBUS (or any other digital IO pin) must not be more than $V_{IO} + 2.5V$.

If you had a 1.8V controller connected to the CP2102N, then IO set IO voltage to 1.8V. VBUS being fed directly from USB will go over absolute maximum specs given in Table 3.10.

So you should be alright without divider if you are using the CP2102N with 5V and 3.3V logic levels and always powered on (as is the case with ESP32 chips).

Also, the CP2102-GMR datasheet explains it better. The resistor divider prevents problems when V_{IO} is 0 but VBUS is still present... because max VBUS will be 2.5V if $V_{IO} = 0V$. Hope that helped!



PORTFOLIO

SERVICES

ARTICLES ▾

NEWS

ABOUT US



CONTACT US
LINKEDIN



STORE
EMAIL



GI

DISCLAIMER: The information provided on this website is for informational use only. PCB Artists provides
@2021 - All Right Reserved. Designed and Developed by P

Store Terms and Conditions • Privacy Policy

^
BACK TO TOP